



Lesson 19 – QUESTIONS

- Q1 Why does an Op amp have a + Vin and a -Vin?
- Q2 What are the two golden rules when using Op amps?
- Q3 What is an open and closed loop amplifier?
- Q4 What is Common Mode rejection?
- Q5 What is EMI?
- Q6 What is EMC?
- Q7 What is an example of a natural EMI in a receiver?
- Q8 What are the four basic methods for eliminating the effects of EMI on a system?

