



## Lesson 6

# CAPACITORS AND INDUCTORS

ACMA Syllabus February 2024 Chapters 2.2 and 2.3

### Contents

|                                    |    |
|------------------------------------|----|
| Capacitors.....                    | 2  |
| Capacitor sizes.....               | 2  |
| Symbols.....                       | 3  |
| Types of capacitors.....           | 3  |
| Dielectric Loss.....               | 4  |
| Charge .....                       | 4  |
| Capacitor Voltage and Current..... | 5  |
| Series RC Circuit .....            | 6  |
| Capacitor in series.....           | 7  |
| Capacitors in parallel.....        | 8  |
| Quality Factor .....               | 8  |
| Reactance.....                     | 8  |
| Inductors.....                     | 10 |
| Inductor sizes .....               | 10 |
| Symbols.....                       | 10 |
| Types of Inductors.....            | 11 |
| Energy.....                        | 11 |
| Voltage and Current.....           | 11 |
| Series RL Circuit .....            | 13 |
| Inductor in Series.....            | 14 |
| Inductors in Parallel.....         | 14 |
| Quality Factor .....               | 14 |
| Reactance.....                     | 15 |

## Capacitors


A capacitor is a two-terminal component that can store electrical energy in an electric field by accumulating charge on two closely spaced parallel conductive plates. These plates are separated by an insulator called a dielectric.

If a voltage potential is placed across these plates, the plates will achieve the same voltage as the power source. If the voltage source is removed. The capacitor will retain the charge and discharge over time. A capacitor blocks DC current.

The capacitance is dependent several factors.

- The plate sizes (A).
- The plate separation (d)
- The dielectric material between the plates. Dielectrics can be any material such as paper, air, plastic, etc.

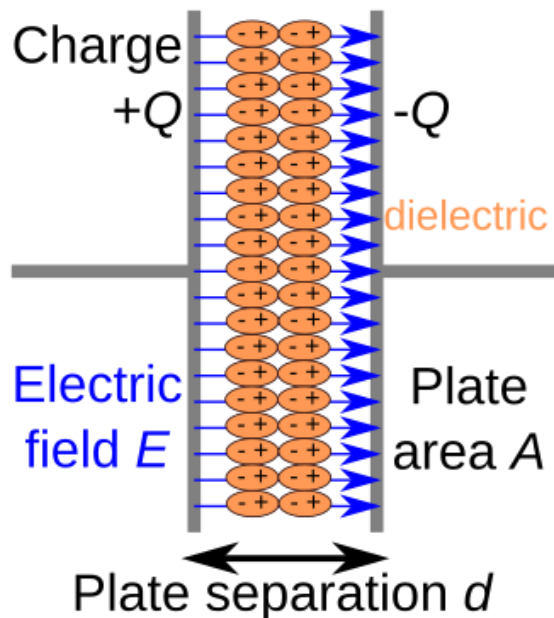
Capacitors are measured in Farads (F) named after the English physicist and chemist Michael Faraday. Most common capacitors are measured in microfarads ( $\mu\text{F}$ ) or picofarads (pF)



### Capacitor sizes

| Prefix Name | Abbreviation  | Weight            | Equivalent Farads |
|-------------|---------------|-------------------|-------------------|
| Picofarad   | pF            | 10 <sup>-12</sup> | 0.000000000001 F  |
| Nano farad  | nF            | 10 <sup>-9</sup>  | 0.000000001 F     |
| Microfarad  | $\mu\text{F}$ | 10 <sup>-6</sup>  | 0.000001 F        |
| Millifarad  | mF            | 10 <sup>-3</sup>  | 0.001 F           |

## Symbols

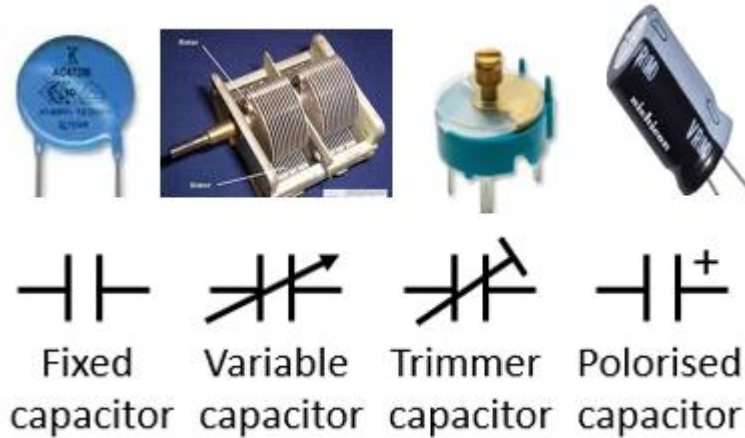

- A fixed capacitor has a predefined capacitance.
- A variable capacitor can be mechanically or electronically changed over a predefined range of capacitance.
- A trimmer capacitor is a set and forget device. The capacitor has a small range, and once set is not altered.
- A polarised capacitor is used for high capacitance values in power filtering and energy storage.

**WARNING:** If a polarised capacitor is connected to the incorrect polarity, the capacitor may heat up and leak or explode.

## Types of capacitors

**Ceramic capacitors** – A ceramic capacitor is a fixed-value capacitor where the ceramic material is the dielectric. Two or more alternating layers of ceramic and a metal layer act as the electrodes. Ceramic capacitors can be used as a general-purpose capacitor, since they are not polarized.



**Electrolytic capacitors** - Electrolytic capacitors are polarized and must be connected to the voltage supply correctly. An electrolytic capacitor uses an oxide film made of aluminium, tantalum or other oxidizable metal as a dielectric. This type of capacitor is used extensively in power supply circuits and similar applications.



**Film capacitors -**

Most common capacitor and are non-polarized. Polypropylene (PP) film capacitors are used for high-frequency high-power applications such as induction heating, pulsed power energy discharge applications and as AC capacitors for electrical distribution. The AC voltage ratings of these capacitors can range up to 400 kV.



**Variable capacitors -**

The capacitance is variable through a defined range.



**Dielectric Loss**

Dielectric loss is the loss of energy in heating a dielectric material in a varying electric field between two plates of the capacitor.

**Charge**

Capacitance is a measure of its ability to hold a charge in Coulombs.

The capacitance formula is:

$$C = \frac{Q}{V}$$

C is the capacitance Farads.

Q is the magnitude of the charge in Coulombs.

V is the potential difference across the circuit element in volts.

**Example:** What is the size of the capacitor if the voltage is 50 mV and 5 micro coulombs of charge?

$$C = \frac{0.000005}{0.05}$$

$$C = 0.1 \text{ mF}$$

**Example:** What is the charge on the 5µF capacitor if the voltage is 12V?

$$Q = C \times V$$



$$Q = 0.000005 \times 12$$

$$Q = 60 \mu \text{ coulombs}$$
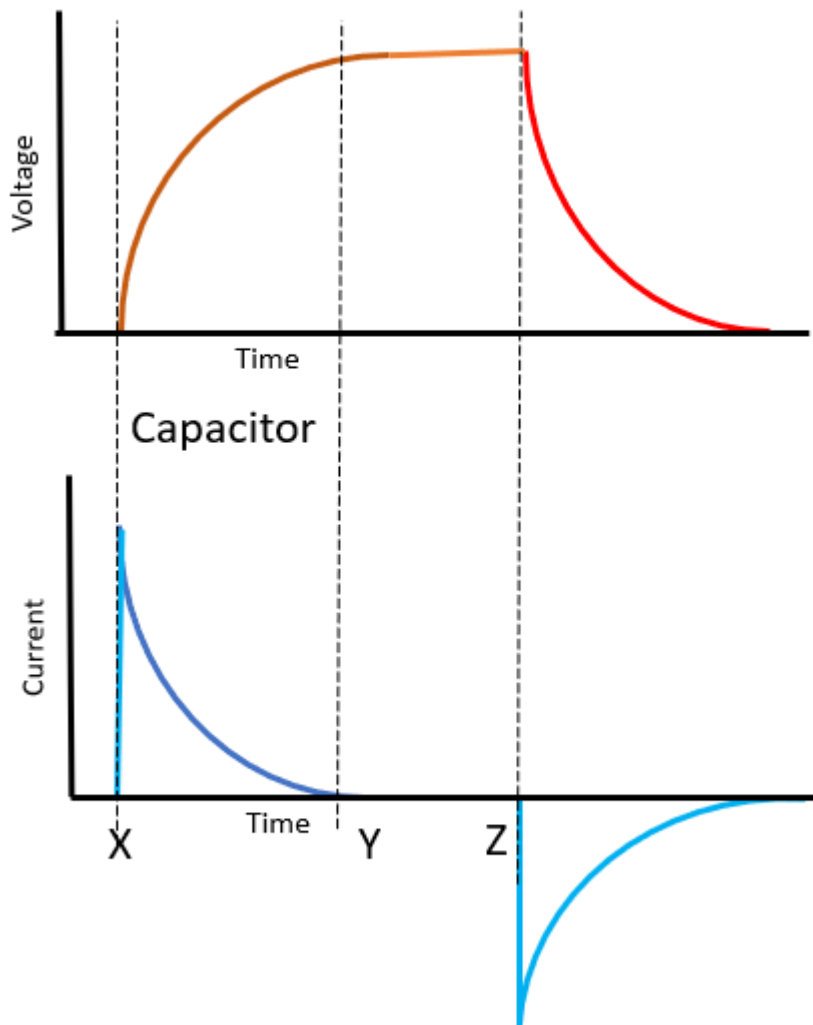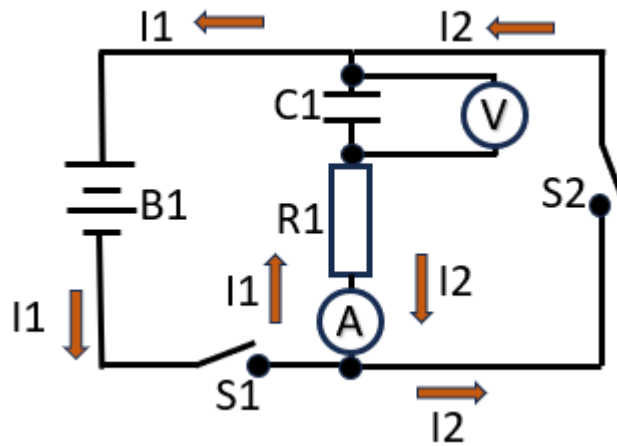
### Capacitor Voltage and Current

When a voltage is placed across a capacitor, the capacitor will charge to the applied voltage. A resistor is used to control the current flow when charging and discharging the capacitor. The charging and discharging times for combination of the capacitor and resistor can be calculated.

Looking at the circuit below, the capacitor and resistor are in the circuit with a battery, ammeter and voltmeter.



**NOTE:** The timeline X, Y and Z may be in microseconds.

### Close S1 at time X (Capacitor charging)

Electrons will flow anticlockwise (I1) and deposit electrons on the bottom side of the capacitor. This makes the bottom side of the capacitor negative compared to the top side. The capacitor will charge, between time X and Y, and when the capacitor is charged, the electron flow will stop. The capacitor blocks DC. The ammeter will rise quickly then taper off. The voltmeter will rise to the charged voltage.

### Open S1 at time Y

The capacitor will retain the charge but will eventually discharge over an extended time.

### Close S2 at time Z (Capacitor discharging)

As the capacitor was charged and the bottom side is now negative, the current will flow in the opposite direction (E2). The voltage and current will drop to zero.


See the graphs below to demonstrate this charging and discharging.

A good video demonstrating this effect can be seen [HERE](#).
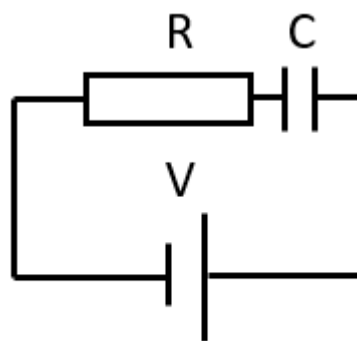
### Series RC Circuit

A resistor (R) and capacitor (C) in series, the capacitor charges until the voltage across the capacitor is equal to the supply voltage (V).

The time for this charging can be determined and controlled. Capacitor charging was covered in lesson 6.



Series RC circuit

Figure 1

The time, in seconds, for the capacitor to charge depends on the resistor in Ohms and capacitor in Farads.

The time constant of a series RC circuit, denoted by the Greek letter tau ( $\tau$ ), represents the time required for a capacitor to charge to approximately **63.2%** of its final supply voltage or discharge to approximately **36.8%** of its initial voltage. It is a measure of how quickly the circuit responds to changes in voltage.

$$\tau = C \times R$$

$\tau$  = Time in seconds (Greek letter Tau)

R = Resistance in ohms.

C = Capacitance in Farads


**Example:** A 6 uF capacitor with a 1 M $\Omega$  resistor is connected to a 12 V DC supply. What is the charge time?

$$\begin{aligned}\tau &= C \times R \\ &= 0.000006 \times 1,000,000 \\ &= 6 \text{ Seconds}\end{aligned}$$
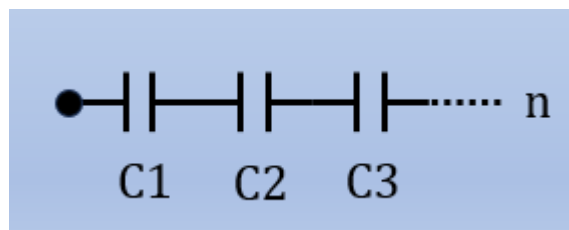
### Capacitor in series

Capacitors in **series** are treated the same way as resistors in **parallel**.

$$\frac{1}{C_t} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \dots n$$




**Example:** The capacitors in series are 3mF, 6mF and 9 mF what is the total capacitance?

$$\begin{aligned}1/C_t &= 1 / 0.003 + 1 / 0.006 + 1 / 0.009 \\ 1/C_t &= 333.33 + 166.66 + 111.11 \\ 1/C_t &= 611.1 \\ C_t &= 0.0016 \text{ F or } 1.6 \text{ mF}\end{aligned}$$

### Capacitors in parallel

Capacitors in **parallel** are treated the same way as resistors in **series**.

$$C_t = C_1 + C_2 + C_3 \dots n.$$

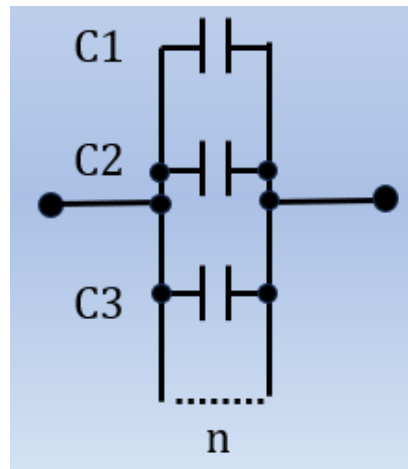

**Example:** The capacitors in parallel are 3mF, 6mF and 9 mF what is the total capacitance?

$$C_t = 0.003 + 0.006 + 0.009$$

$$C_t = 0.018 \text{ F or } 180 \text{ mF}$$

### Quality Factor

A capacitor's Quality Factor is its efficiency by comparing the energy stored to the energy dissipated as heat. A **high-Quality factor** indicates **low losses**.

### Reactance

The capacitor's opposition to alternating current is called Reactance. Reactance is symbolized by the capital letter "X" and is measured in ohms.

At DC, the capacitor resistance is infinitely high. As the frequency increases, the reactance of the capacitor to the AC signal decreases.

Capacitive reactance is  $X_c$ .

- Low frequencies – High  $X_c$
- High frequencies – Low  $X_c$

The capacitive reactance can be calculated with the formula.

$$X_c = \frac{1}{2\pi f C}$$

$X_c$  = Capacitive reactance in Ohms

f = frequency in hertz (Hz)

C = capacitance in Farads

$\pi$  = 3.141 (Pi)

**Example:** What is the reactance of a 300mf capacitor at 1kHz?

$$X_c = \frac{1}{2\pi fC}$$

$$X_c = \frac{1}{2 \times 3.141 \times 1000 \times 0.3}$$

$$X_c = \frac{1}{1884}$$

$$X_c = 5 \text{ ohms}$$

## Inductors

An inductor is made with insulated wire wound into a coil. Sometimes called a coil, choke, or reactor.

The inductor stores energy in a magnetic field when electric current flows through it.

The inductance (L) of the device is measured in Henrys (H), named after Joseph Henry. A Henry is the amount of inductance that generates one voltage when the current is changing at a rate of one ampere per second.

An inductor inhibits AC current.

The inductance of a coil depends on several factors.

- Coil diameter.
- Cross sectional area
- Number of turns
- Type of material at the core.




### Inductor sizes

| Prefix Name | Abbreviation | Weight | Equivalent Henrys |
|-------------|--------------|--------|-------------------|
| Pico Henry  | pH           | 10-12  | 0.000000000001 H  |
| Nano Henry  | nH           | 10-9   | 0.000000001 H     |
| Micro Henry | μH           | 10-6   | 0.000001 H        |
| Milli Henry | mH           | 10-3   | 0.001 H           |

### Symbols

Inductor symbols are shown below.

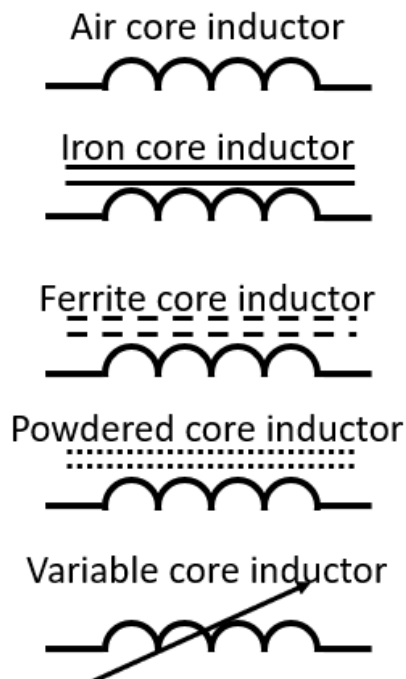

### Types of Inductors

- Air-Core Inductors –** These inductors are open coil offering low inductance making them ideal for high-frequency (RF) applications.
- Ferrite-Core Inductors-** Inductor core is ferromagnetic material for high permeability and high inductance. These inductors are suitable for high-frequency, low-loss applications.
- Iron-Core Inductors -** Iron or steel cores are used for high-inductance, low-frequency, and high-power applications.
- Powdered Iron Core Inductors –** The inductor core is iron powder to store more energy and features low eddy current losses.
- Variable Inductors-** Can change inductance over a defined range.

### Energy

The energy stored in an inductor is measured in Joules. Energy is related to the current and the inductance.

$$W = \frac{I^2 \times L}{2}$$

W = Energy in Joules

I = current in amperes

L = inductance in Henries



**Example:** How much energy is stored in a 5H inductor fed by 2 A of current?

$$W = \frac{I^2 \times L}{2}$$
$$W = \frac{2^2 \times 5}{2}$$
$$W = \frac{20}{2}$$
$$W = 10 \text{ Joules}$$
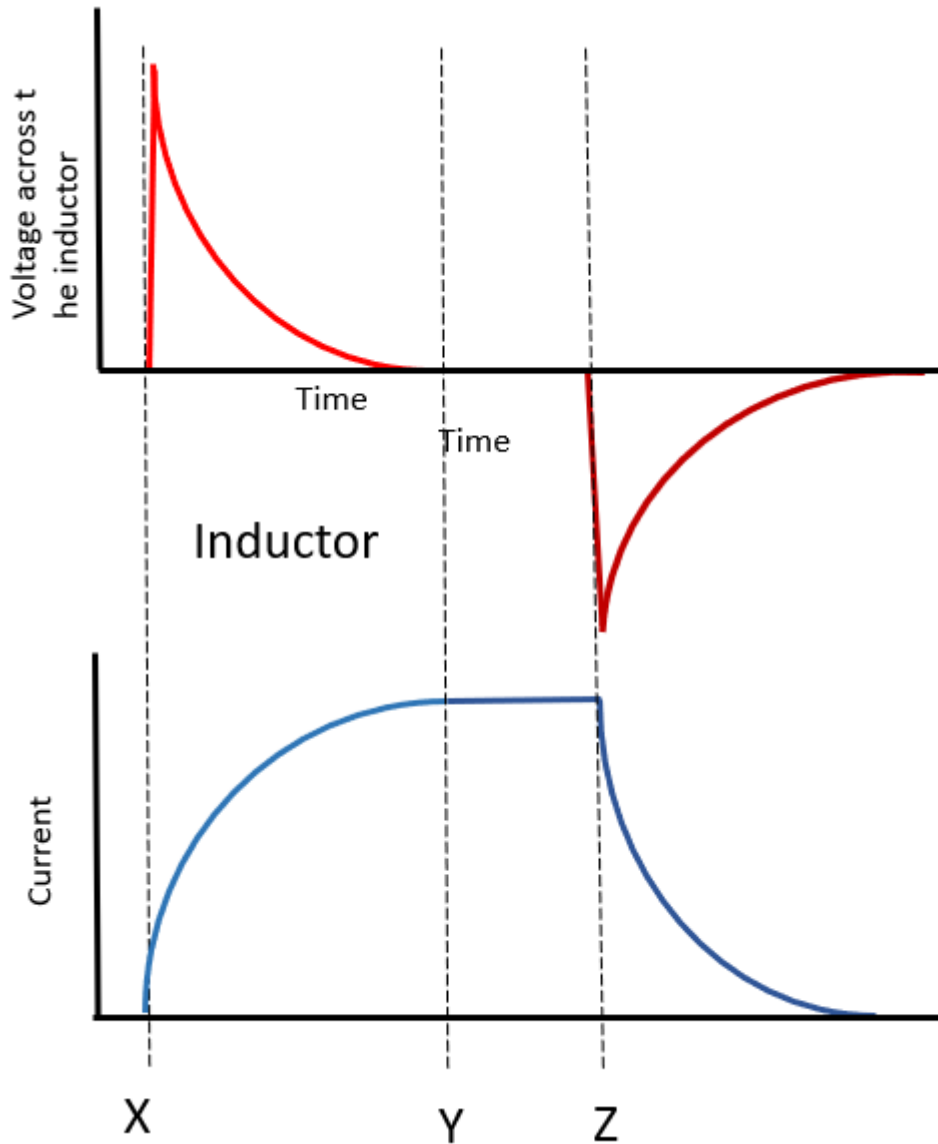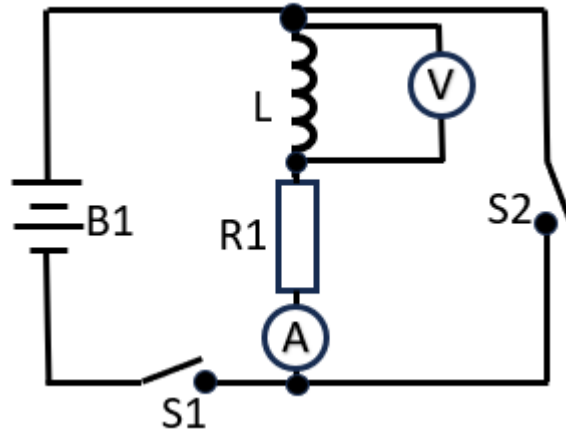
### Voltage and Current

Current passed through an inductor will generate a magnetic field around the inductor. A resistor is used to control the current flow when charging and discharging an inductor.

Looking at the circuit below, the inductor and resistor are in the circuit with a battery, ammeter and voltmeter.



**NOTE:** The timeline X, Y and Z may be in microseconds.

### Close S1 at time X

The initial flow of current will generate a magnetic field in the inductor, and a self-induced voltage will initially resist any change. (Lenz's Law) At this time, the inductor will present as a high resistance and the voltage of B1 will be seen across the voltmeter. As the current reaches a steady state at point Y, the magnetic flux will remain steady and the resistance across the inductor will approach zero. No voltage drop will be measured across the inductor.

### Time Y to Z

The current remains at a steady state as the inductor does not block DC.


### Open S1 and Close S2 at time Z

As the current flow drops, the magnetic flux will collapse causing a back EMF voltage in the opposite direction. This will then taper off as the current flow stops.

**WARNING:** The back EMF can generate large voltages.
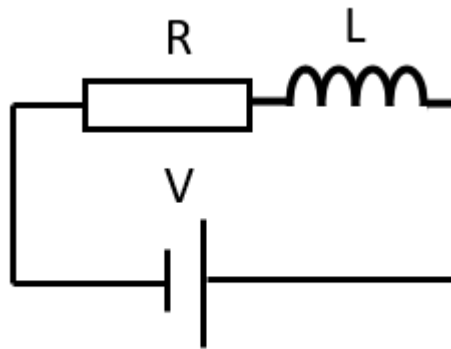
### Series RL Circuit

If a resistor and inductor are connected in series, the self-inductance of the coil will resist the current flow as the magnetic field is generated. Once the field reaches its peak only the resistor will limit current flow. The time for the field to generate can be calculated.



Series RL circuit

Time in seconds, resistance in Ohms and inductance in Henries.

$$\tau = \frac{L}{R}$$

$\tau$  = Time in seconds (Greek letter Tau)

R = Resistance in ohms.

L = Inductance in Henrys

**Example:** 1kΩ resistor, 140 mH inductor and V of 12 V.

$$\begin{aligned} \tau &= \frac{L}{R} \\ &= \frac{0.140}{1000} \\ &= 14 \text{ microseconds.} \end{aligned}$$

### Inductor in Series

Inductors in **series** are the same as resistors in **series**.

$$L_t = L_1 + L_2 + L_3 \dots n$$




**Example:** Three inductors in series, a 3mH, 5 mH and 10 mH. What is the total inductance?

$$\begin{aligned} L_t &= 3 + 5 + 10 \\ L_t &= 18 \text{ mH} \end{aligned}$$
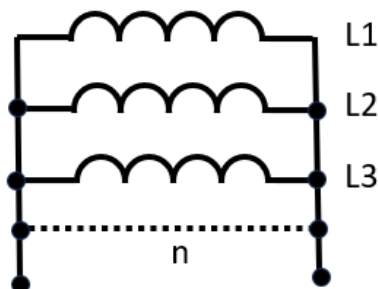
### Inductors in Parallel

Inductors in **parallel** are the same as resistors in **parallel**.

$$\frac{1}{L_t} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \dots n$$



**Example:** Three inductors in parallel, a 3mH, 5 mH and 10 mH. What is the total inductance?

$$\begin{aligned} 1/L_t &= 1/3 + 1/5 + 1/10 \\ 1/L_t &= 0.33 + 0.2 + 0.1 \\ 1/L_t &= 0.63 \\ L_t &= 1.58 \text{ mH} \end{aligned}$$

### Quality Factor

The quality factor (or Q) of an inductor is the ratio of its inductive reactance to its resistance at a given frequency and is a measure of its efficiency. The higher the Q factor of the inductor, the closer it approaches the behaviour of an ideal inductor.

### Reactance

An inductor has a DC resistance in the wire measured in Ohms.

The inductor's opposition to alternating current is called Reactance. Reactance is symbolized by the capital letter "X" and is measured in ohms just like resistance (R).

Inductive reactance is  $X_L$ .

An inductor passes low frequencies and presents a high reactance to high frequencies.

As the frequency increases, the reactance of the inductor to the AC signal also increases.

- Low frequencies – Low  $X_L$
- High frequencies – High  $X_L$

$$X_L = 2 \times \pi \times f \times L$$

$X_L$  = Inductor reactance in Ohms

f = frequency in hertz (Hz)

L = Inductance in Henries

$\pi$  = 3.141 (Pi)

**Example:** What is the reactance of a 2mH inductor at 1MHz?

$$X_L = 2 \times 3.141 \times 1000000 \times 0.002$$

$$X_L = 12,564 \text{ ohms or } 12.564\text{k Ohms}$$

Go to Lesson 6 Questions.

